
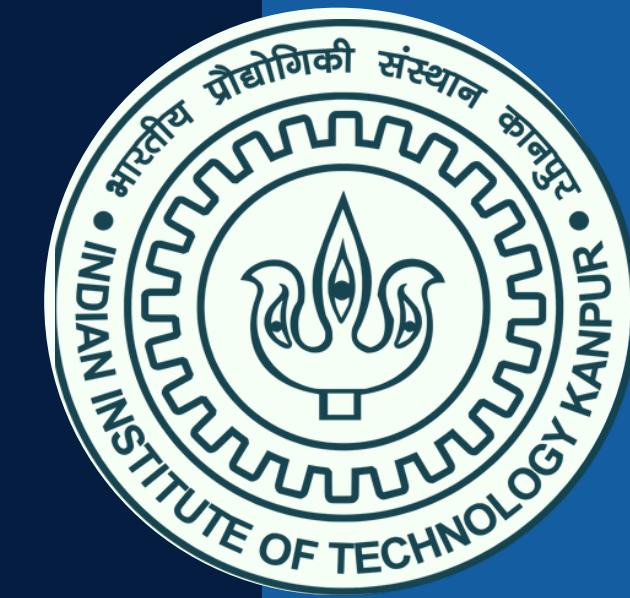


*Electrical  
Engineering  
Association*

# DIGI WARE PROJECT

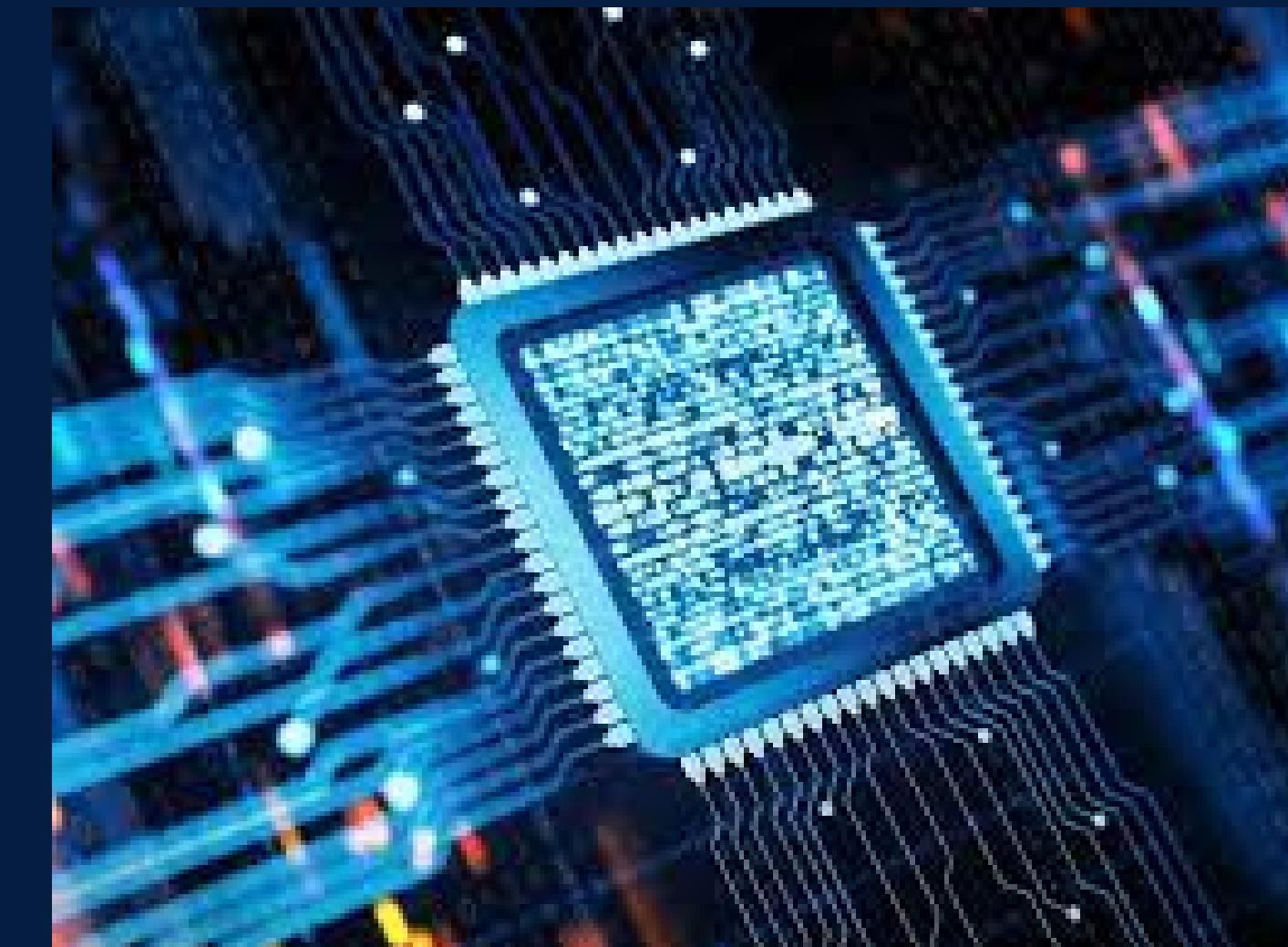

# OUR TEAM

**Ayan  
Gupta**

---

220258

**Saladi  
Teja Sri**

---

220941

**Sukhadia  
Patil**

---

220761

**Pranshu  
Thirani**

---

220801

**Arpita  
Chaurasia**

---


220207

## MENTORS:

- Meenakshi Mondal
- Shreeja Mantapuram
- Adrija Bera



# SCIENTIFIC CALCULATOR

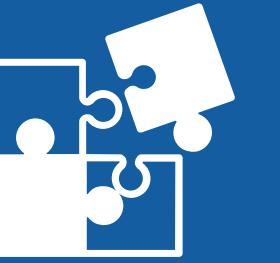

## PROBLEM STATEMENT

Design a basic calculator which takes two single-digit numbers (each is a single-digit decimal base number entered by user) as input and can perform unsigned addition, subtraction, multiplication and division (only quotient) based on user selection and display the output decimal number (two digits) to the user .




# OBJECTIVES

**O1** To design a basic CALCULATOR which takes two single digit numbers as input.

**O2** The calculator should perform the desired operation(among addition,subtraction,multiplication,division).

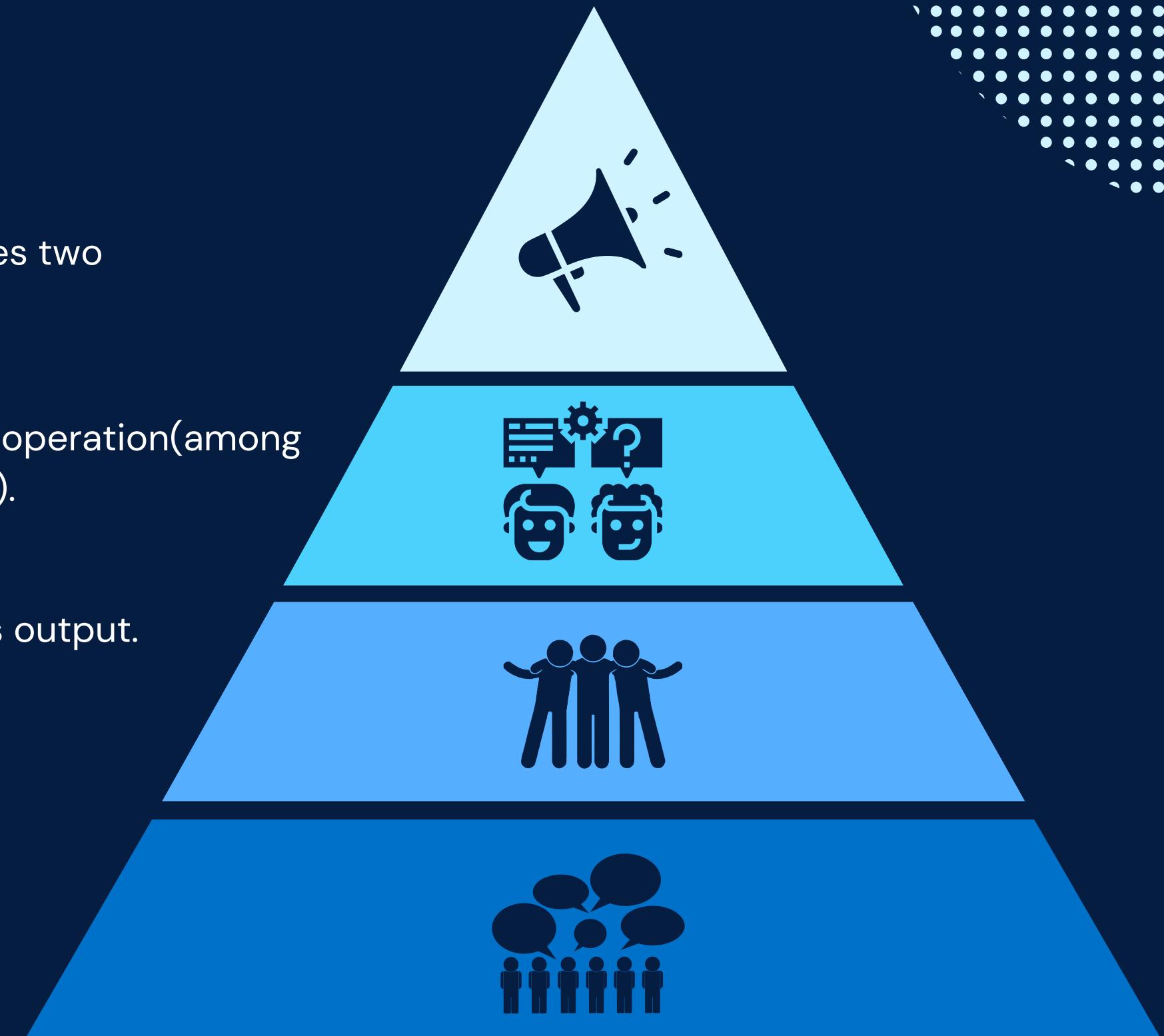**O3** It should give two digit decimal number as output.



# Cracking the Nut of the Module

---

- Module name: calc

Inputs:

- en: Enable signal (active high)
- in1: First operand (4-bit)
- in2: Second operand (4-bit)
- ops: Operation selector (2-bit)

Outputs:

- total: Result of the calculation (8-bit)

# Test bench

---

- Module name: calc\_tb

## Inputs:

- en: Enable signal (active high)
- in1: First operand (4-bit)
- in2: Second operand (4-bit)
- ops: Operation selector (2-bit)

## Outputs:

- total: Result of the calculation (8-bit)

Test cases for each of the operations-addition, subtraction, multiplication and division are created and tested

# Cracking the Nut of the Module

---

- Module name: add

Inputs:

- in1: First operand (4-bit)
- in2: Second operand (4-bit)

Outputs:

- out: Result of addition (8-bit)

# Cracking the Nut of the Module

---

- Module name: multiply

Inputs:

- in1: First operand (4-bit)
- in2: Second operand (4-bit)

Outputs:

- out: Result of multiplication (8-bit)

# Cracking the Nut of the Module

---

- Module name: sub

Inputs:

- in1: First operand (4-bit)
- in2: Second operand (4-bit)

Outputs:

- out: Result of subtraction (8-bit)

# Cracking the Nut of the Module

---

- Module name: div

Inputs:

- in1: First operand (4-bit)
- in2: Second operand (4-bit)

Outputs:

- out: Result of division (8-bit)

# WAVEFORM

en is high(active)



Operation(ops)

0

1

2

3

Output(total)

Addition

Subtraction


Multiplication

Division

Displaying Output in the Hexadecimal System

# WAVEFORM

en is high(active)

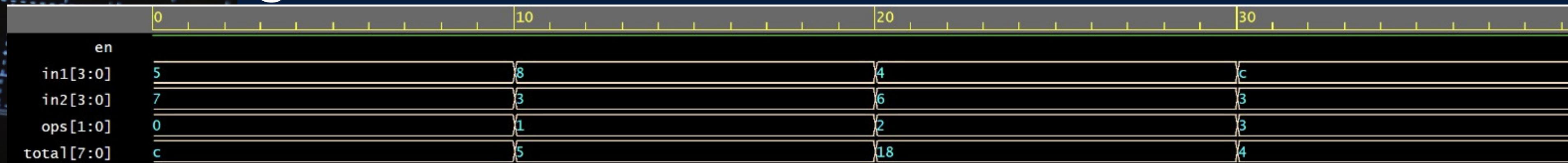

Duration of Wave Form: 0 seconds to 40 seconds.

# WAVEFORM

en is low(inactive)



*Inactivity of the system results in zero output,  
regardless of the input, when the enable(en) is low.*

Duration of Wave Form: 0 seconds to 40 seconds.

Thank You !!